

Index Number – 210098R

Name – De Silva A.P.C.

Assigned Task –

Understanding the concepts and then designing & developing a 2 to 4 decoder.

Then Designing and developing a 3 to 8 decoder using 2 to 4 decoders.

After that, designing and developing 8 to 1 multiplexer using a 3 to 8 decoder after properly identifying the relevant logic circuit.

(Verification of the specific functionalities through simulations is included in each one of them.)

VHDL codes –

Decoder_2_to_4.vhd

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 03/21/2023 09:43:25 PM  
-- Design Name:  
-- Module Name: Decoder_2_to_4 - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:
```

-- Revision 0.01 - File Created

-- Additional Comments:

--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity Decoder_2_to_4 is

Port (I : in STD_LOGIC_VECTOR (1 downto 0);

EN : in STD_LOGIC;

Y : out STD_LOGIC_VECTOR (3 downto 0));

end Decoder_2_to_4;

architecture Behavioral of Decoder_2_to_4 is

begin

Y(0)<= not I(0)and not I(1)and EN;

Y(1)<= not I(1)and I(0)and EN;

Y(2)<= I(1)and not I(0)and EN;

Y(3)<= I(0)and I(1)and EN;

end Behavioral;

TB_Decoder_2_to_4.vhd

-- Company:

-- Engineer:

--

-- Create Date: 03/22/2023 12:10:51 AM

```
-- Design Name:
-- Module Name: TB_Decoder_2_to_4 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

```
entity TB_Decoder_2_to_4 is
-- Port ( );
end TB_Decoder_2_to_4;
```

```
architecture Behavioral of TB_Decoder_2_to_4 is
COMPONENT Decoder_2_to_4
    PORT( I : in STD_LOGIC_VECTOR (1 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR (3 downto 0));
END COMPONENT;
    signal IO,I1 : STD_LOGIC ;
    signal Y0,Y1,Y2,Y3 : STD_LOGIC ;
    signal EN : STD_LOGIC;
begin
    UUT: Decoder_2_to_4 PORT MAP(
    I(0) => IO,
```

```
I(1) => I1,  
Y(0) => Y0,  
Y(1) => Y1,  
Y(2) => Y2,  
Y(3) => Y3,  
EN => EN);
```

```
process
```

```
begin
```

```
    EN <= '0';
```

```
    IO <= '0';
```

```
    I1 <= '0';
```

```
  
    WAIT FOR 100 ns;
```

```
    IO <= '1';
```

```
  
    WAIT FOR 100 ns;
```

```
    IO <= '0';
```

```
    I1 <= '1';
```

```
  
    WAIT FOR 100 ns;
```

```
    IO <= '1';
```

```
  
    WAIT FOR 100 ns;
```

```
    IO <= '0';
```

```
    I1 <= '0';
```

```
    EN <= '1';
```

```
  
    WAIT FOR 100 ns;
```

```
    IO <= '1';
```

```
  
    WAIT FOR 100 ns;
```

```
    IO <= '0';
```

```
    I1 <= '1';
```

```
  
    WAIT FOR 100 ns;
```

```
    IO <= '1';
```

```
    WAIT;
```

```
end process;
```

```
end Behavioral;
```

Decoder_3_to_8.vhd

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 03/22/2023 02:58:34 AM  
-- Design Name:  
-- Module Name: Decoder_3_to_8 - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating  
-- any Xilinx leaf cells in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;
```

```
entity Decoder_3_to_8 is  
    Port ( I : in STD_LOGIC_VECTOR (2 downto 0);  
          EN : in STD_LOGIC;  
          Y : out STD_LOGIC_VECTOR (7 downto 0));  
end Decoder_3_to_8;
```

```
architecture Behavioral of Decoder_3_to_8 is  
    component Decoder_2_to_4
```

```

port(
I: in STD_LOGIC_VECTOR;
EN: in STD_LOGIC;
Y: out STD_LOGIC_VECTOR );
end component;
signal I0,I1 : STD_LOGIC_VECTOR (1 downto 0);
signal Y0,Y1 : STD_LOGIC_VECTOR (3 downto 0);
signal en0,en1, I2 : STD_LOGIC;
begin
Decode_2_to_4_0 : Decoder_2_to_4
port map(
I => I0,
EN => en0,
Y => Y0 );
Decode_2_to_4_1 : Decoder_2_to_4
port map(
I => I1,
EN => en1,
Y => Y1 );
en0 <= NOT(I(2)) AND EN;
en1 <= I(2) AND EN;
I0 <= I(1 downto 0);
I1 <= I(1 downto 0);
I2 <= I(2);
Y(3 downto 0) <= Y0;
Y(7 downto 4) <= Y1;
end Behavioral;

```

TB_Decoder_3_to_8.vhd

```

-----
-- Company:
-- Engineer:
--
-- Create Date: 03/22/2023 03:00:12 AM
-- Design Name:
-- Module Name: TB_Decoder_3_to_8 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--

```

-- Dependencies:

--

-- Revision:

-- Revision 0.01 - File Created

-- Additional Comments:

--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity TB_Decoder_3_to_8 is

-- Port ();

end TB_Decoder_3_to_8;

architecture Behavioral of TB_Decoder_3_to_8 is

COMPONENT Decoder_3_to_8

PORT(I : in STD_LOGIC_VECTOR (2 downto 0);

EN : in STD_LOGIC;

Y : out STD_LOGIC_VECTOR (7 downto 0));

END COMPONENT;

signal I0,I1,I2 : STD_LOGIC ;

signal Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7 : STD_LOGIC ;

signal EN : STD_LOGIC;

begin

UUT: Decoder_3_to_8 PORT MAP(

I(0) => I0,

I(1) => I1,

I(2) => I2,

Y(0) => Y0,

Y(1) => Y1,

Y(2) => Y2,

Y(3) => Y3,

Y(4) => Y4,

```
Y(5) => Y5,  
Y(6) => Y6,  
Y(7) => Y7,  
EN => EN);
```

```
process
```

```
begin
```

```
    EN <= '0';  
    I0 <= '0';  
    I1 <= '1';  
    I2 <= '0';  
    WAIT FOR 100 ns;  
    I2 <= '1';
```

```
  
    WAIT FOR 100 ns;
```

```
    I0 <= '1';
```

```
    I2 <= '0';
```

```
    WAIT FOR 100 ns;
```

```
    EN <= '1';
```

```
    I0 <= '0';
```

```
    I2 <= '0';
```

```
    WAIT FOR 100 ns;
```

```
    I2 <= '1';
```

```
  
    WAIT FOR 100 ns;
```

```
    I0 <= '1';
```

```
    I2 <= '0';
```

```
  
    WAIT FOR 100 ns;
```

```
    I0 <= '1';
```

```
    I1 <= '0';
```

```
    I2 <= '1';
```

```
  
    WAIT;
```

```
end process;
```

```
end Behavioral;
```


Mux_8_to_1.vhd

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 03/22/2023 01:32:17 PM  
-- Design Name:  
-- Module Name: Mux_8_to_1 - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating  
-- any Xilinx leaf cells in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;
```

```
entity Mux_8_to_1 is  
  Port ( S : in STD_LOGIC_VECTOR (2 downto 0);  
        D : in STD_LOGIC_VECTOR (7 downto 0);  
        EN : in STD_LOGIC;  
        Y : out STD_LOGIC);  
end Mux_8_to_1;
```

```
architecture Behavioral of Mux_8_to_1 is
```

```

component Decoder_3_to_8
port(
I: in STD_LOGIC_VECTOR;
EN: in STD_LOGIC;
Y: out STD_LOGIC_VECTOR );
end component;
signal Decoder_in : STD_LOGIC_VECTOR(7 downto 0);
begin
Decode_3_to_8_0 : Decoder_3_to_8
port map(
    I => S,
    EN => EN,
    Y => Decoder_in
);
Y <= (D(0) and Decoder_in(0)) or
      (D(1) and Decoder_in(1)) or
      (D(2) and Decoder_in(2)) or
      (D(3) and Decoder_in(3)) or
      (D(4) and Decoder_in(4)) or
      (D(5) and Decoder_in(5)) or
      (D(6) and Decoder_in(6)) or
      (D(7) and Decoder_in(7));

end Behavioral;

```

TB_Mux_8_to_1.vhd

```

-- Company:
-- Engineer:
--
-- Create Date: 03/22/2023 02:21:05 PM
-- Design Name:
-- Module Name: TB_Mux_8_to_1 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--

```

```
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
```

```
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

```
entity TB_Mux_8_to_1 is
-- Port ( );
end TB_Mux_8_to_1;
```

```
architecture Behavioral of TB_Mux_8_to_1 is
COMPONENT Mux_8_to_1
    PORT( S : in STD_LOGIC_VECTOR (2 downto 0);
          D : in STD_LOGIC_VECTOR (7 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC);
END COMPONENT;
```

```
signal S0,S1,S2 : STD_LOGIC ;
signal D0,D1,D2,D3,D4,D5,D6,D7 : STD_LOGIC ;
signal EN,Y : STD_LOGIC;
begin
```

```
UUT: Mux_8_to_1 PORT MAP(
S(0) => S0,
S(1) => S1,
S(2) => S2,
D(0) => D0,
D(1) => D1,
D(2) => D2,
D(3) => D3,
```

```
D(4) => D4,  
D(5) => D5,  
D(6) => D6,  
D(7) => D7,  
Y=>Y,  
EN => EN);
```

```
process
```

```
begin
```

```
    EN <= '0';  
    S0 <= '0';  
    S1 <= '1';  
    S2 <= '0';  
    D0 <= '0';  
    D1 <= '1';  
    D2 <= '0';  
    D3 <= '0';  
    D4 <= '1';  
    D5 <= '1';  
    D6 <= '1';  
    D7 <= '1';
```

```
    WAIT FOR 100 ns;  
    S2 <= '1';
```

```
    WAIT FOR 100 ns;  
    S0 <= '1';  
    S2 <= '0';
```

```
    WAIT FOR 100 ns;  
    EN <= '1';  
    S0 <= '0';
```

```
    WAIT FOR 100 ns;  
    S2 <= '1';
```

```
    WAIT FOR 100 ns;  
    S0 <= '1';  
    S2 <= '0';
```

```
    WAIT FOR 100 ns;  
    S0 <= '0';  
    D2 <= '1';  
    D3 <= '1';
```

```
D6 <= '0';  
D7 <= '0';
```


```
WAIT FOR 100 ns;  
S2 <= '1';
```

```
WAIT FOR 100 ns;  
S0 <= '1';  
S2 <= '0';
```


```
WAIT;  
end process;  
end Behavioral;
```

Design Schematics –


2 to 4 Decoder –

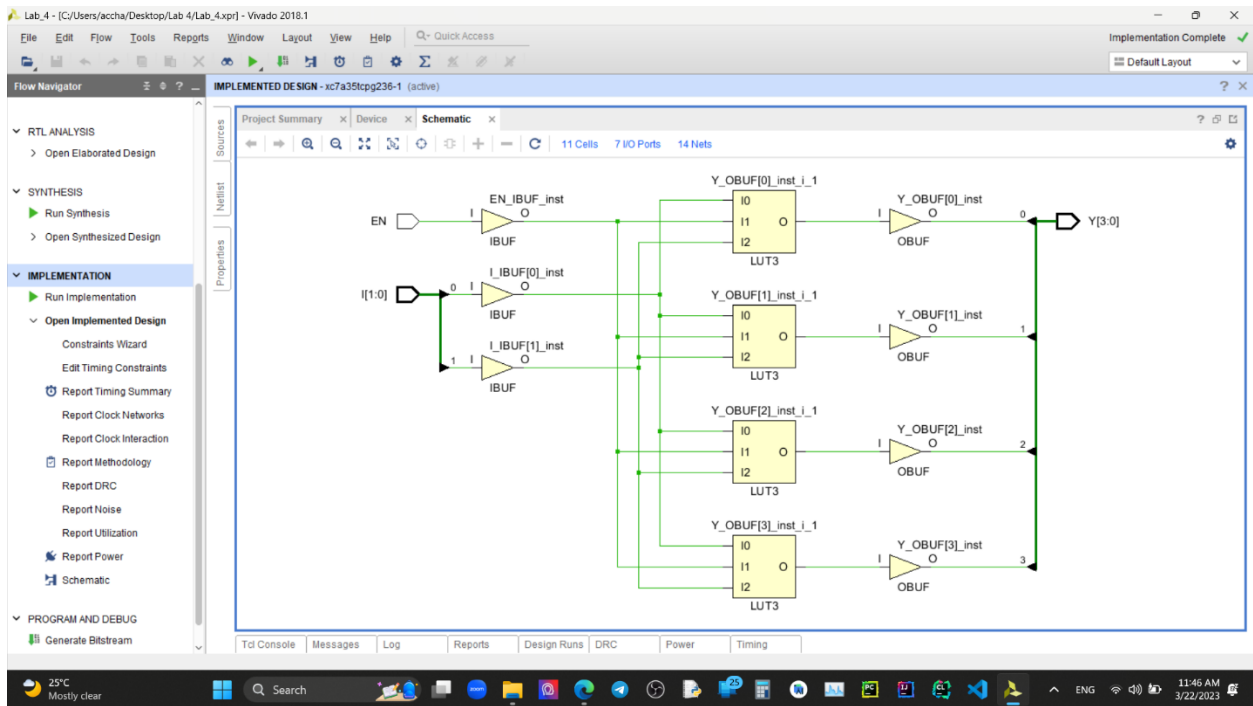

3 to 8 Decoder –

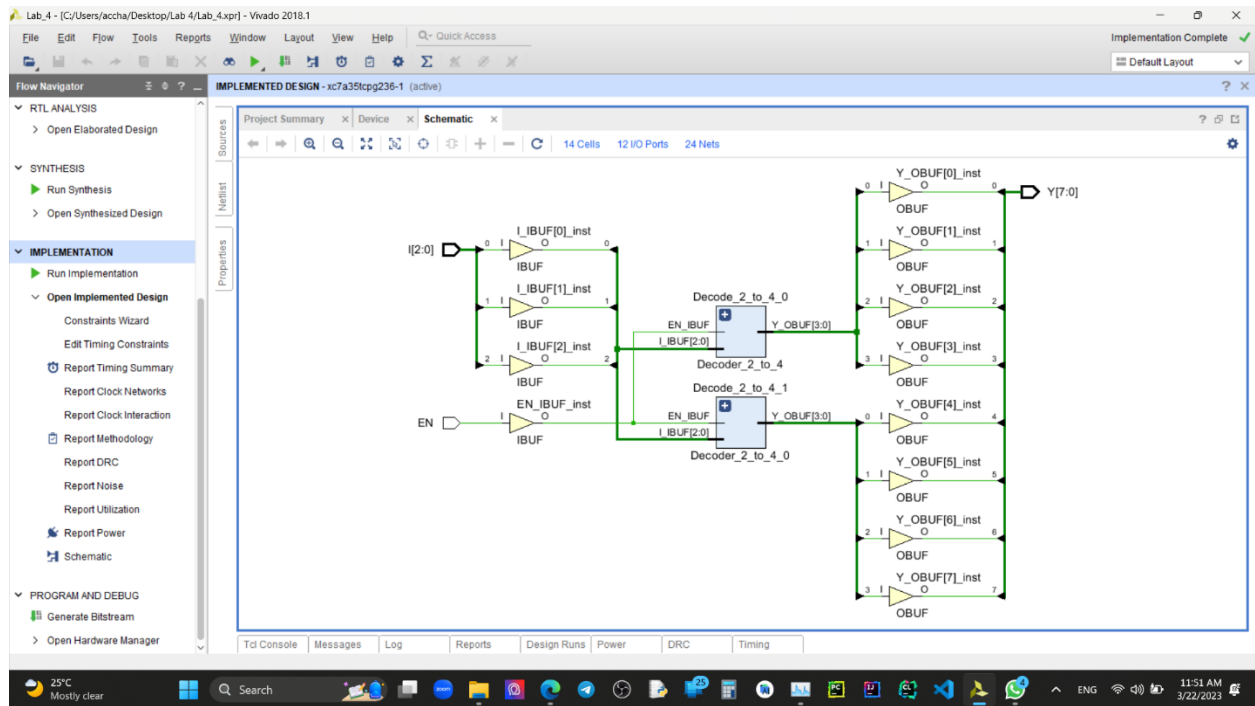


8 to 1 Multiplexer –

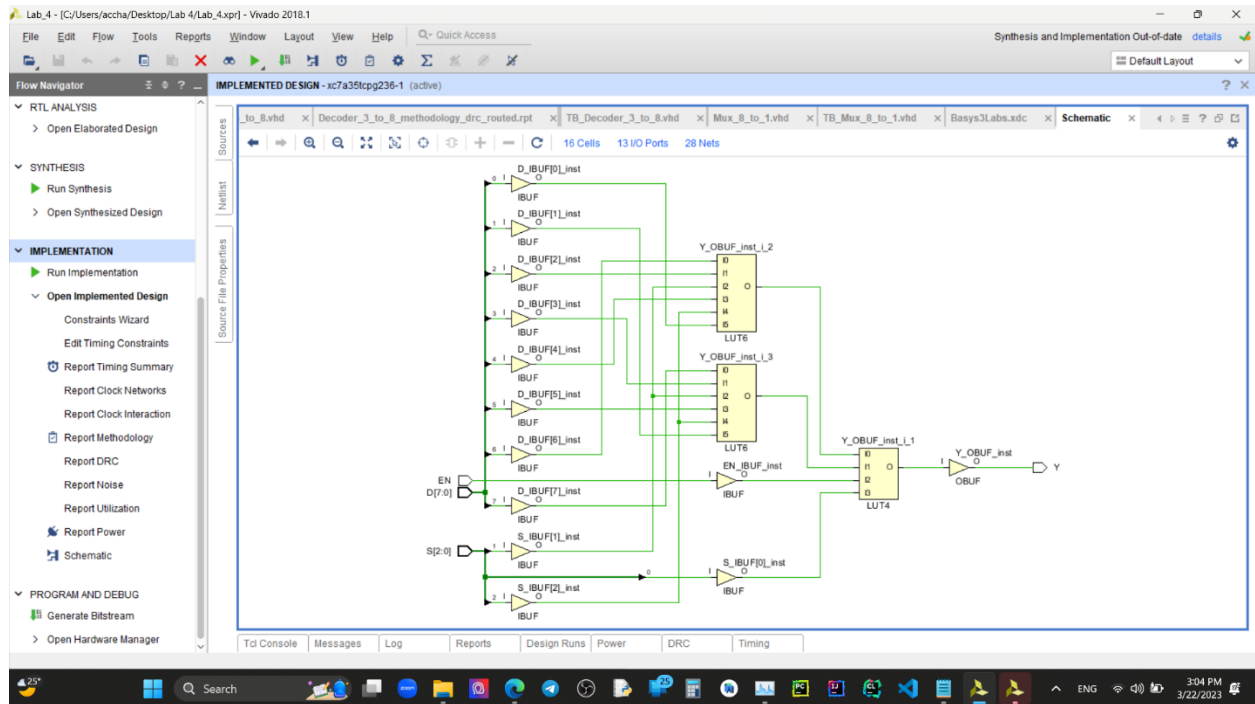


Timing diagrams –


2 to 4 Decoder –

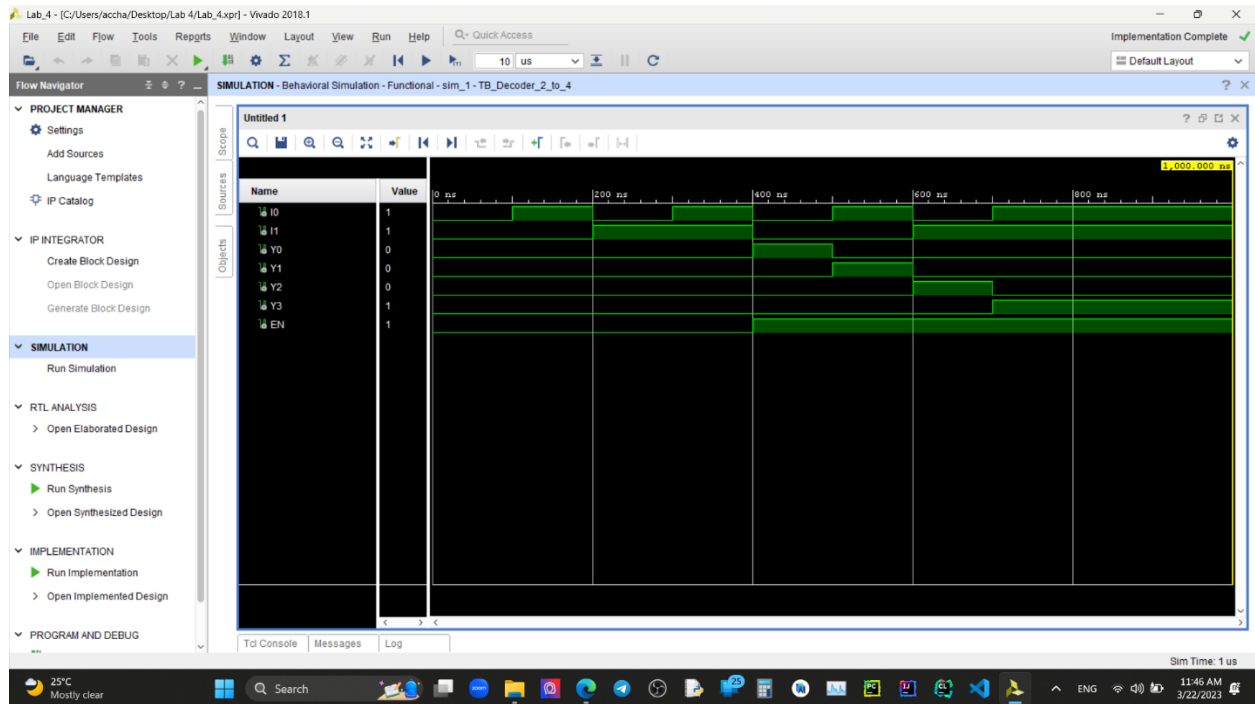

3 to 8 Decoder –

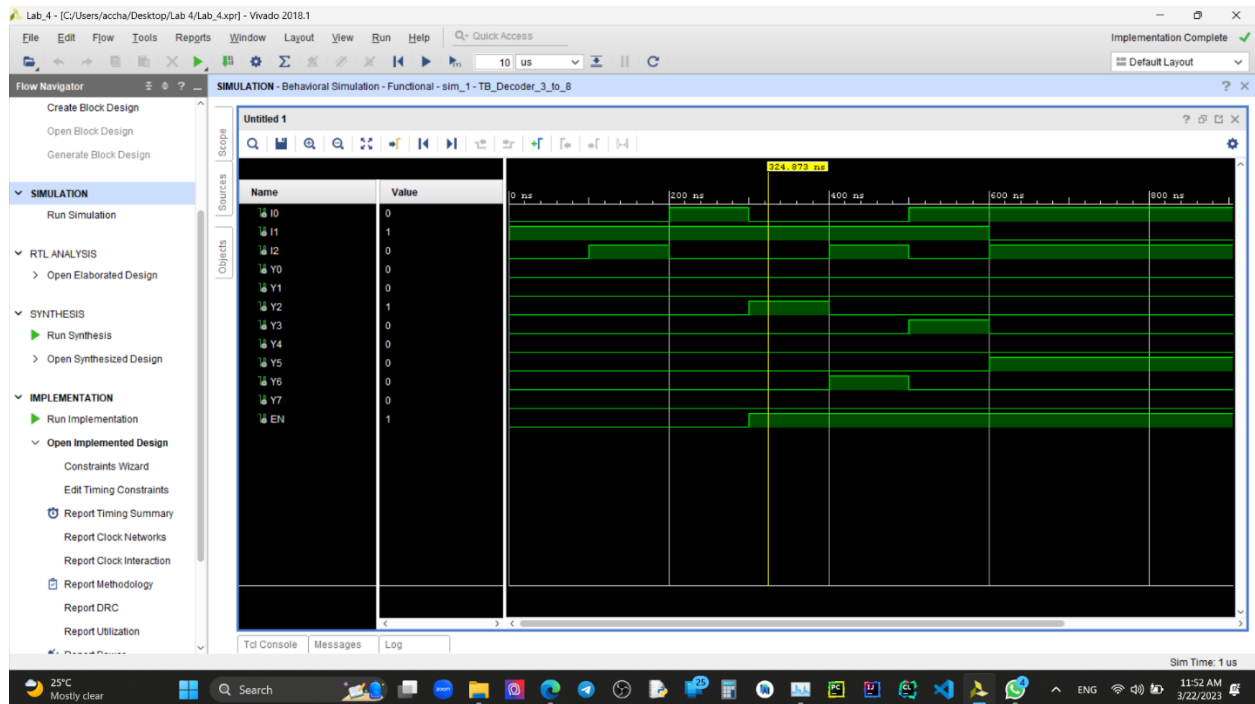

8 to 1 Multiplexer –

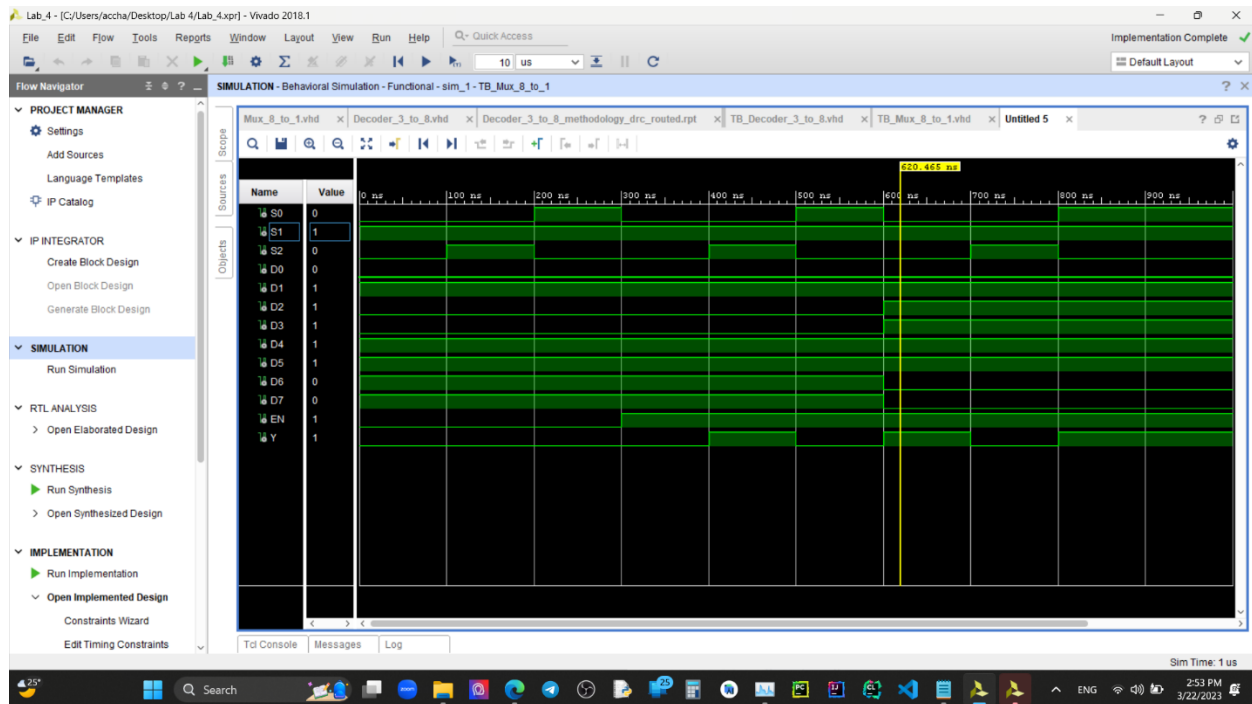

(First En was set to 0 for first 300 ns to check its functionality. Then It was set to 1. In first 600ns, D7 to D0 has values 1 1 1 1 0 0 1 0 respectively and then for the sake of accuracy more tests were done by setting D7 to D0 to values 0 0 1 1 1 1 1 0 . The values of S0-S2 is in the way instructed.)

Conclusion –

Designing a 2 to 4 decoder, then using that decoder to develop a 3 to 8 decoder, and then using the 3 to 8 decoder to design an 8 to 1 multiplexer is a great exercise in comprehending the hierarchical design process in digital logic.

We can create specific components of the circuit that can be reused in larger designs by dividing a complex problem into smaller, more manageable subproblems. This strategy makes it simpler and easier to test and debug the designs while also reducing the complexity of the overall design.